


## Contents :

1. Introduction of Buck-Boost converter
2. Design Specifications of Buck-Boost Converter
  - Assumptions
  - Component Selection
3. Simulation and waveforms of Buck-Boost Converter
4. Conclusion
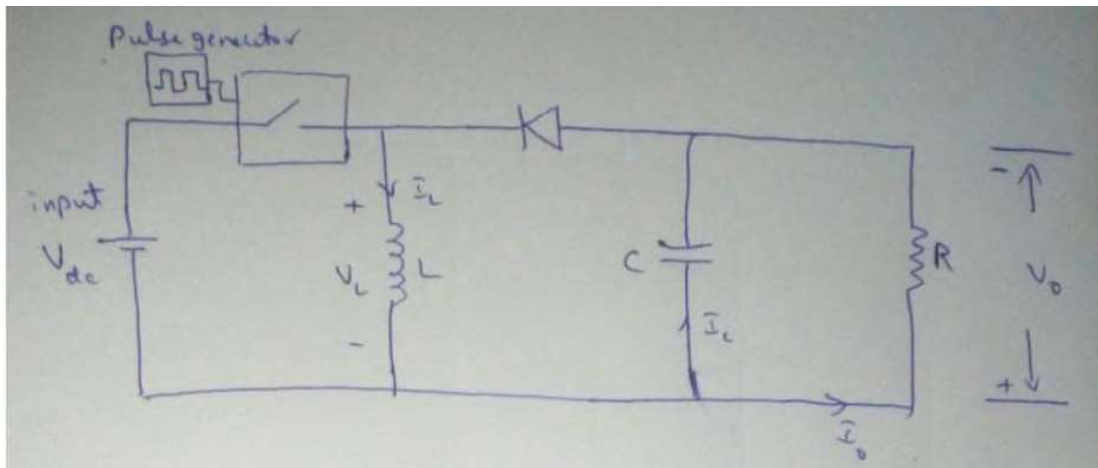
## Introduction : Buck-Boost Converter

- It is a DC-DC converter which produces either a higher output voltage or lower output voltage than the dc input voltage  $V_{dc}$  depending on the duty ratio of the switch.
- It is a cascade connection of two basic DC-DC converters, Buck and Boost Converters.
- It acts as buck converter for  $d < 0.5$  and as boost converter for  $d > 0.5$  and as voltage follower for  $d = 0.5$ .

Below is the basic circuit of a Buck-Boost converter :



- As we know the average voltage across inductor is always zero, hence based on voltage time balance equation we get  $V_o = V_{in} * d / (1-d)$
- As we know the average current through a capacitor is always zero, hence based on current time balance equation we get  $I_o = I_{in} * (1-d) / d$
- The ripple in output current  $\Delta I_L = V_{dc} * d * T / L$
- The ripple in output voltage  $\Delta V_o = I_o * d * T / C$

# Design Specifications:

## Assumptions :

- Assuming input voltage  $V_{dc} = 20V$
- Switching frequency = 5K Hz
- Load Resistance  $R_L = 10 \text{ ohms}$
- Desired permissible Ripple in output current = 0.25 A
- Desired permissible Ripple in output voltage = 0.25 V
- Desired Output voltage :

Case 1 : As Buck converter  $d=0.3$

$$V_o = d * V_{dc} / (1-d)$$

$$V_o = 0.3 * 20 / 0.7$$

$$V_o = 8.57V$$

$$I_o = V_o / R$$

$$I_o = 0.857A$$

Case 2 : As Boost converter  $d=0.7$

$$V_o = d * V_{dc} / (1-d)$$

$$V_o = 0.7 * 20 / 0.3$$

$$V_o = 46.66V$$

$$I_o = V_o / R$$

$$I_o = 4.66A$$

## Component Selection :

1. Switch : For simulation of boost converter we use ideal switch with zero internal resistance and which can operate in high switching frequency
2. Pulse Generator : We need pulse generator to produce gate pulses which can trigger the switch. The Time period of the pulse signals are assumed to be 5K Hz with 30% for buck operation.

3. Inductor : Inductor is chosen based on the permissible ripple allowed in output current.

$$L = V_{dc} * d * T / \Delta I_L$$

Design

For inductor :-  $\Delta I_L = \frac{V_{dc} d T}{L}$

For  $\Delta I_L = 0.25 A \Rightarrow L = \frac{V_{dc} d T}{\Delta I_L} = \frac{20 \times 0.3 \times 0.2 \times 10^{-3}}{0.25}$

$L = 4.8 mH$

4. Capacitor : Capacitor is chosen based on the permissible ripple allowed in output voltage.

$$C = I_o * d * T / \Delta V_o$$

For Capacitor :-  $\Delta V_o = \frac{I_o d T}{C} = \frac{V_o d T}{R C}$

$V_o = \frac{V_{dc} d}{1-d} = \frac{20 \times 0.3}{1-0.3} = 8.57$

$0.25 = \Delta V_o = \frac{8.57 \times 0.3 \times 0.2 \times 10^{-3}}{10 C}$

$C = \frac{8.57 \times 0.3 \times 0.2 \times 10^{-3}}{10 \times 0.25}$

$C = 205.7 \mu F$

# Simulation and waveforms for Buck operation:

Fig 1 : Circuit diagram of a Buck-Boost converter

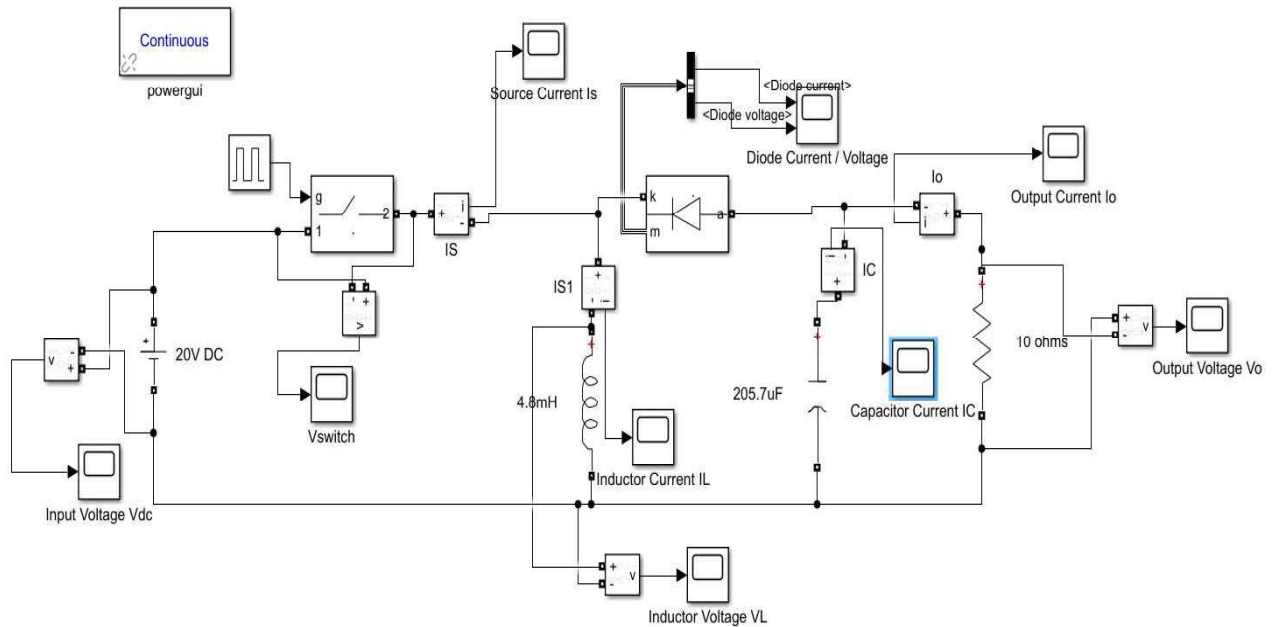


Fig 2 : Input DC Voltage source (Vdc)

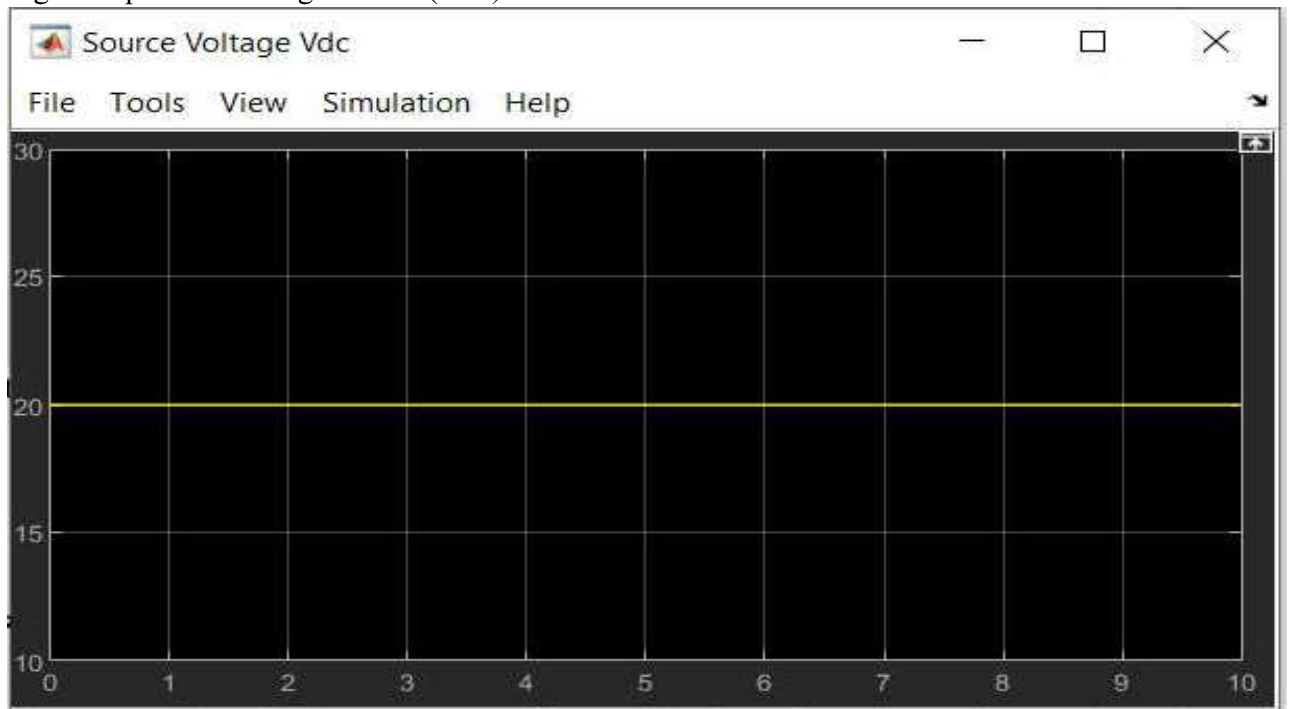


Fig 3 : Source Current waveform / Switch Current  $I_s$

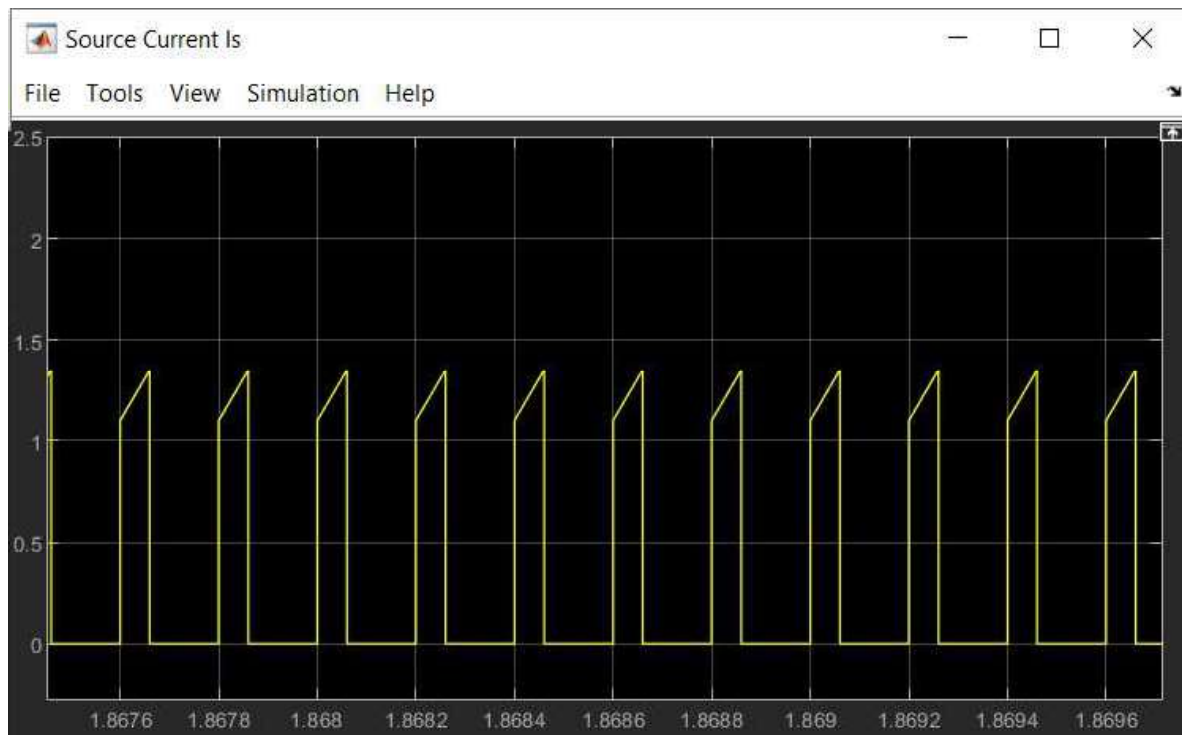


Fig 4 : Output Voltage waveform ( $V_o$ )

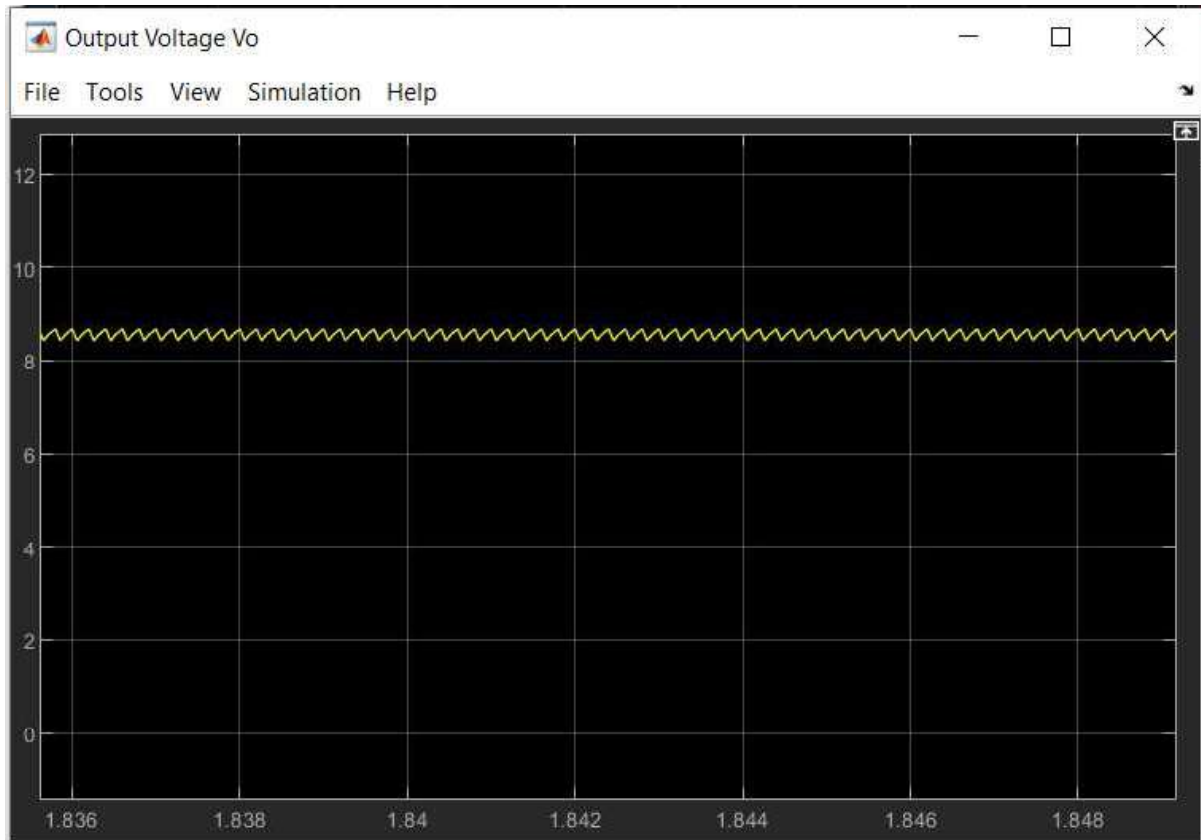


Fig 5 : Output Current waveform ( $I_o$ )

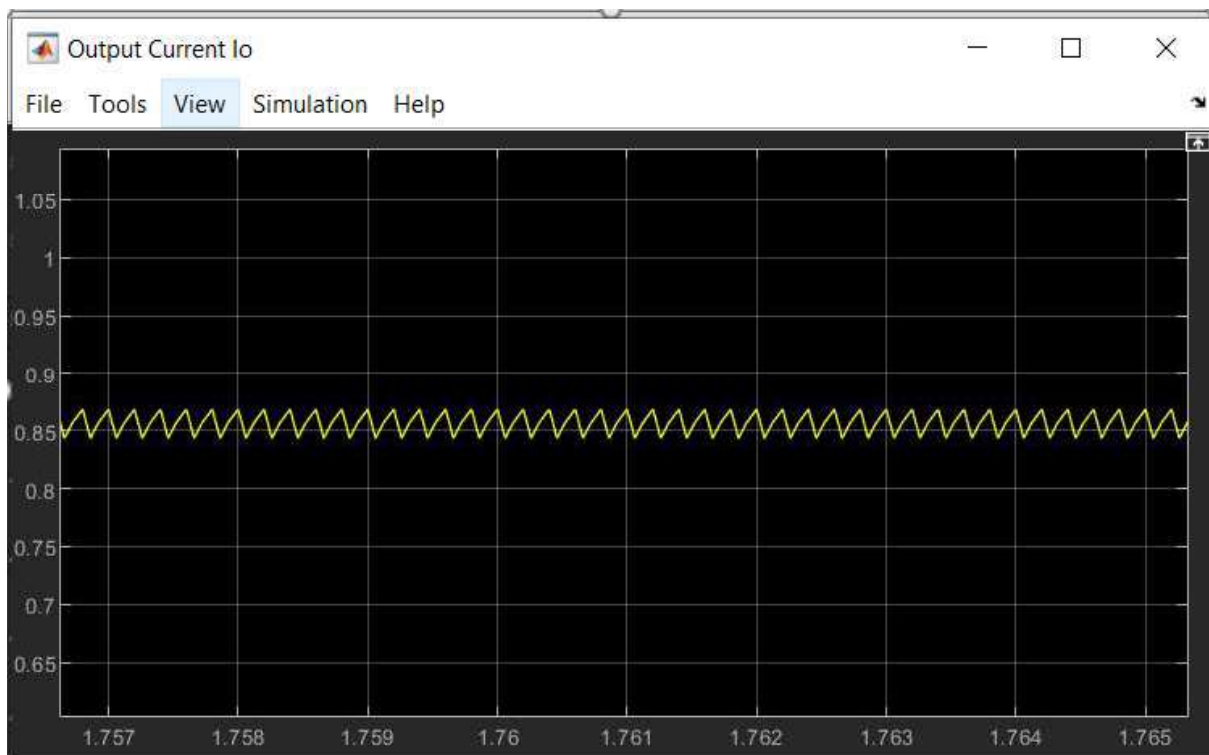


Fig 6 : Voltage across Switch

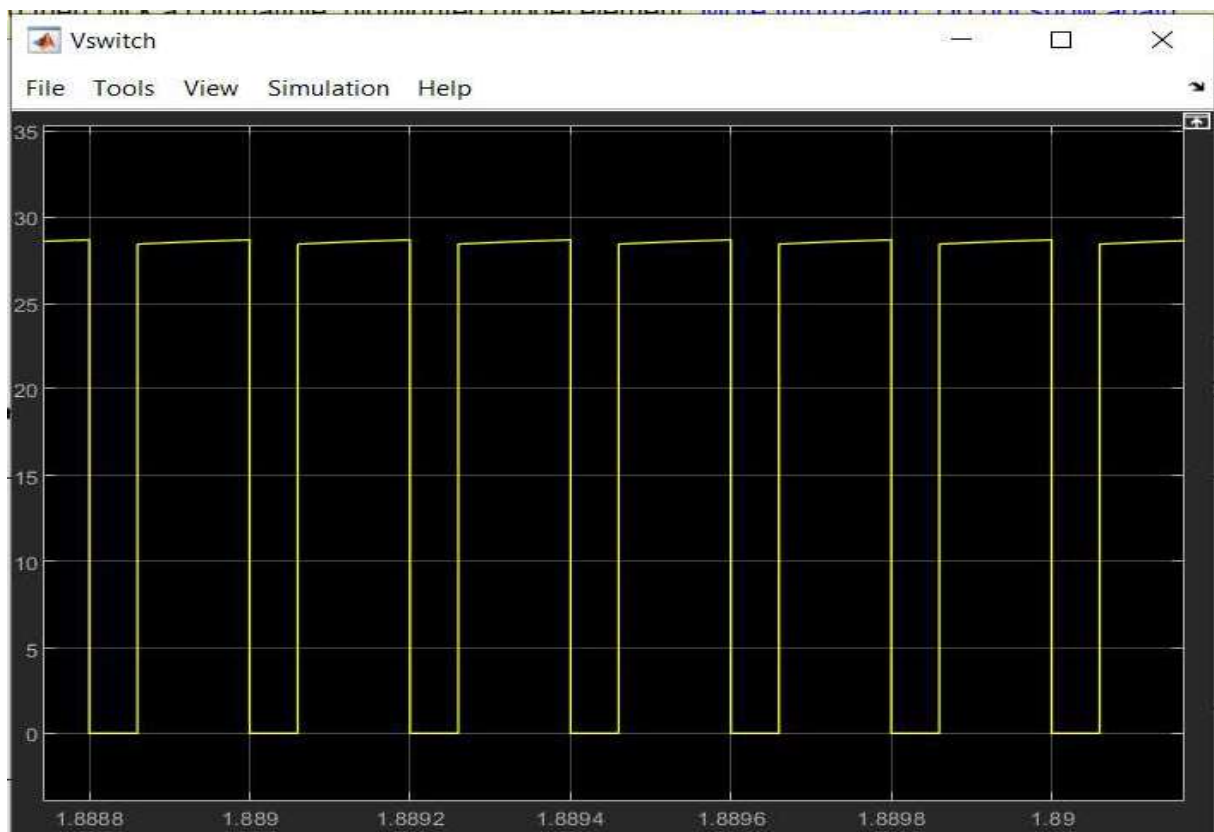


Fig 7 : Voltage across inductor (VL)



Fig 8 : Current through inductor (IL)


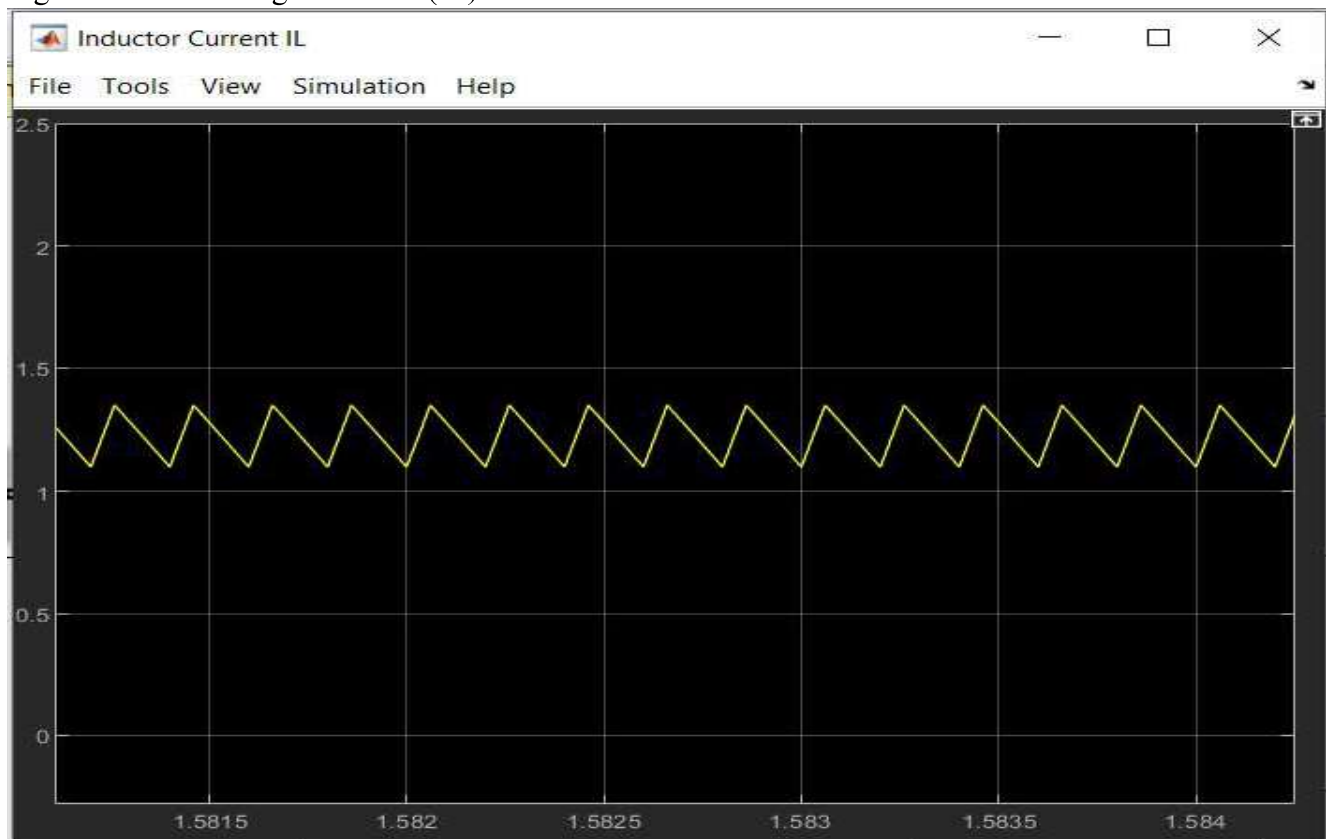


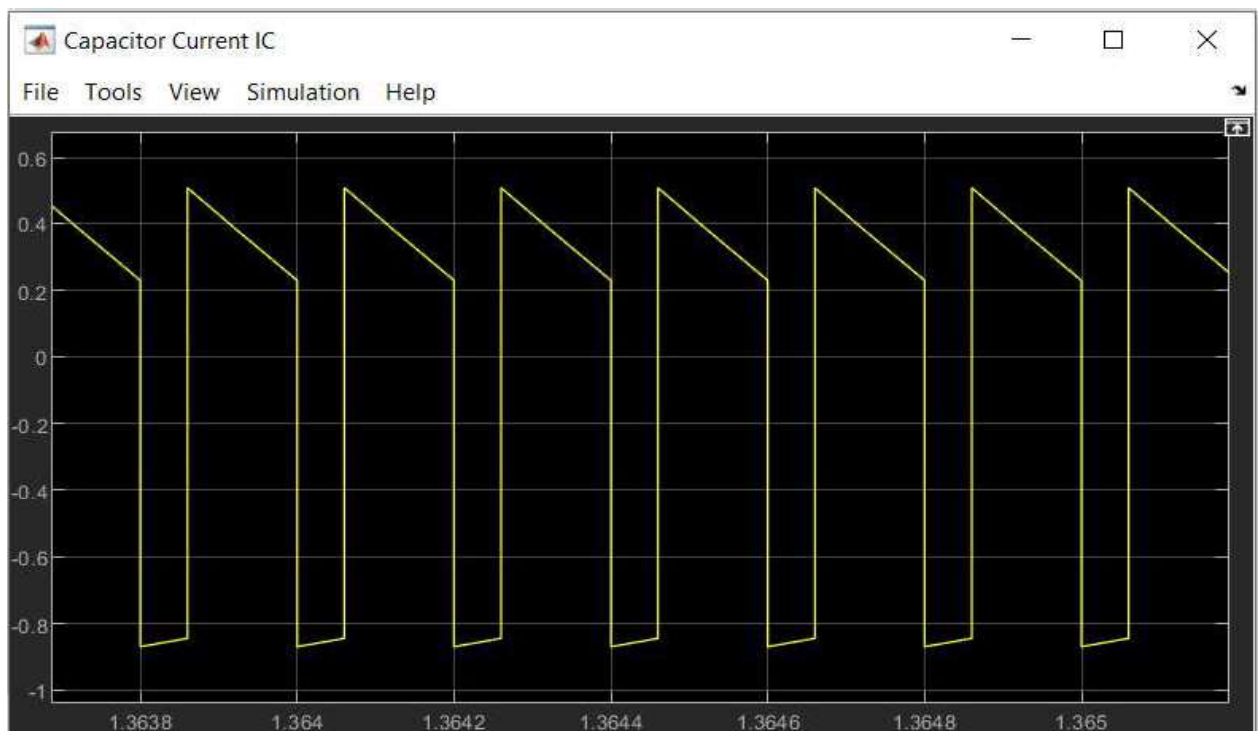

Fig 9 : Current through diode( $I_{\text{diode}}$ ) and Voltage across diode ( $V_{\text{diode}}$ )



Fig 10 : Current through capacitor ( $I_c$ )



Simulation and waveforms for Boost operation:

Fig 2 : Input DC Voltage source ( $V_{dc}$ )

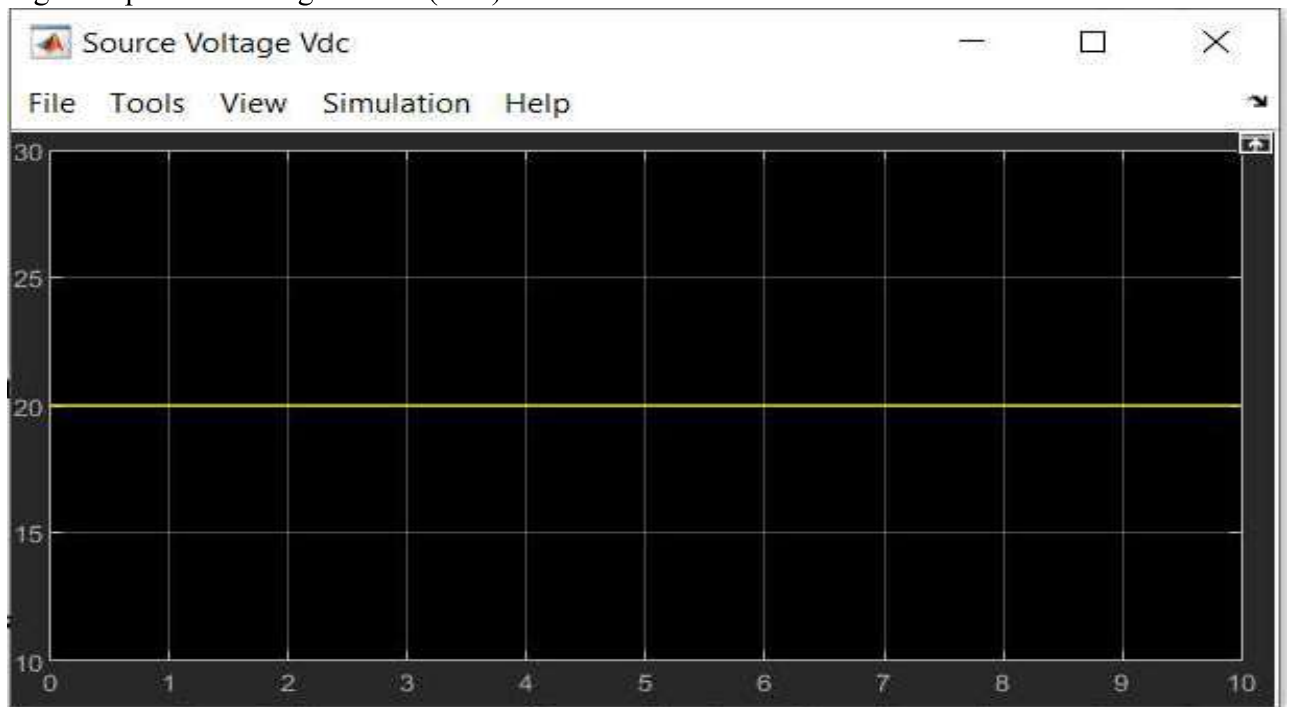


Fig 3 : Source Current waveform / Switch Current  $I_s$

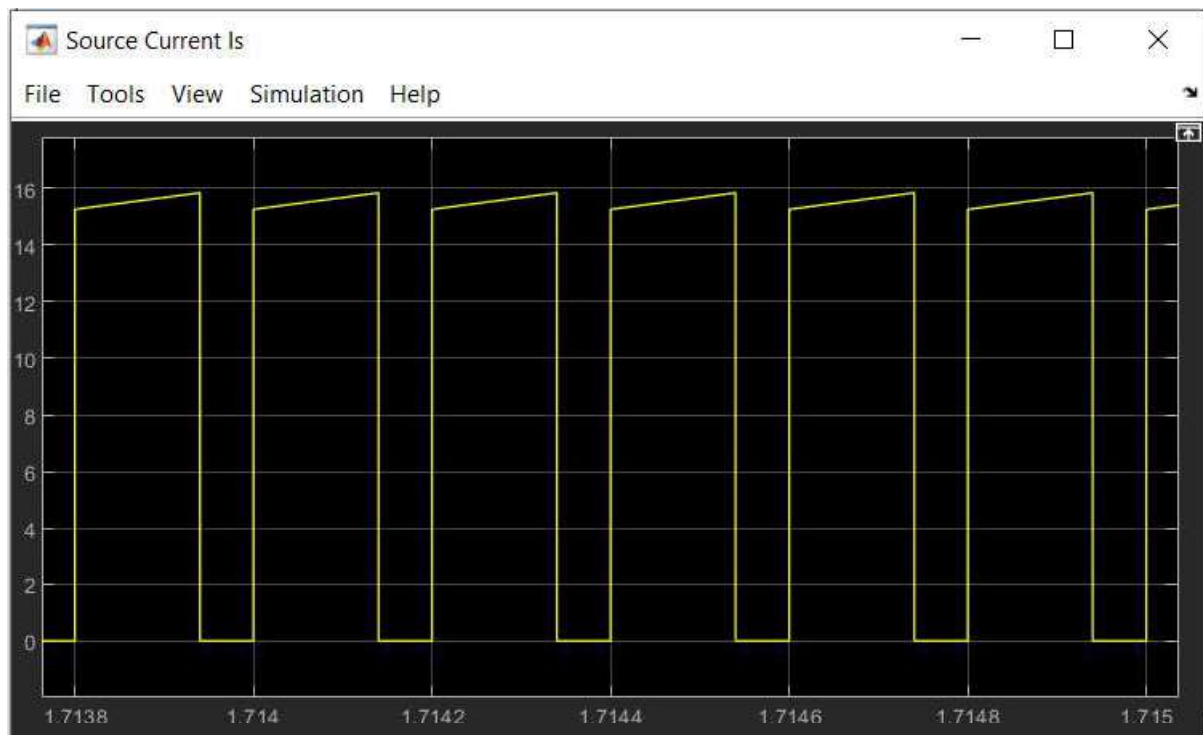


Fig 4 : Output Voltage waveform ( $V_o$ )

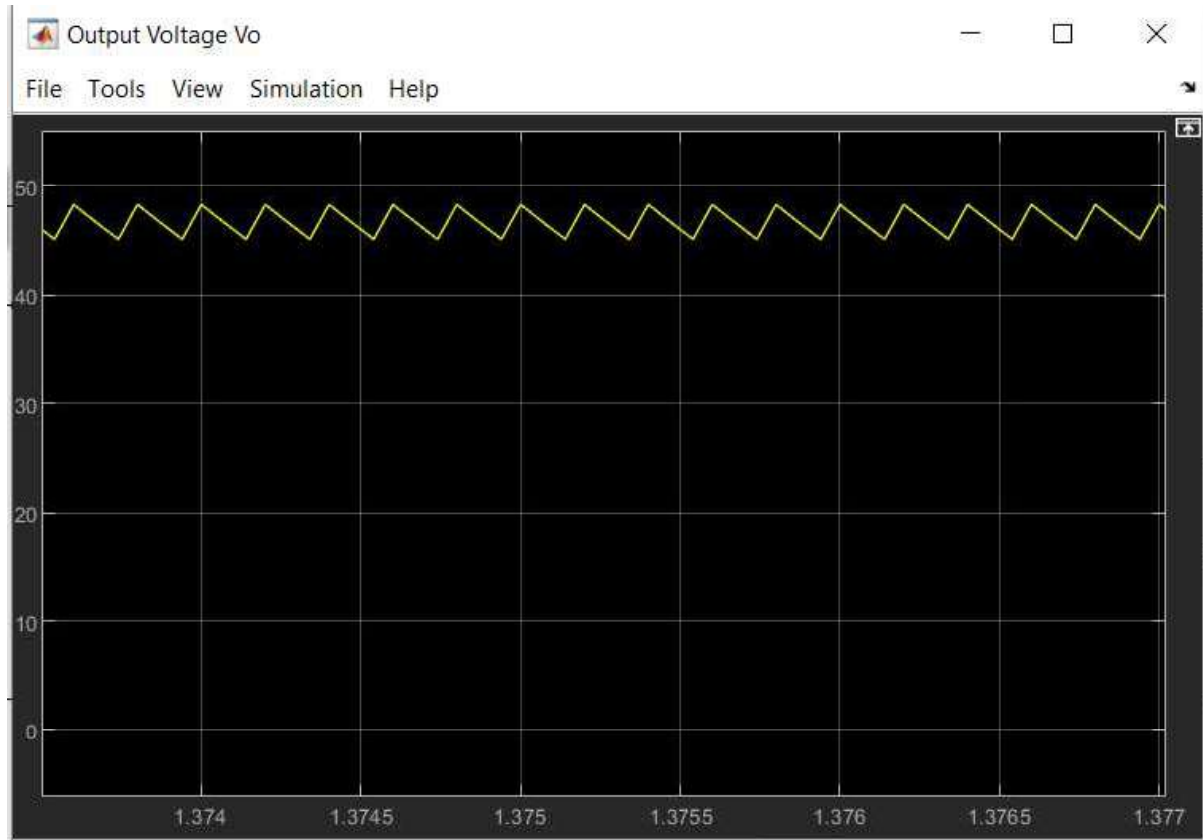


Fig 5 : Output Current waveform ( $I_o$ )

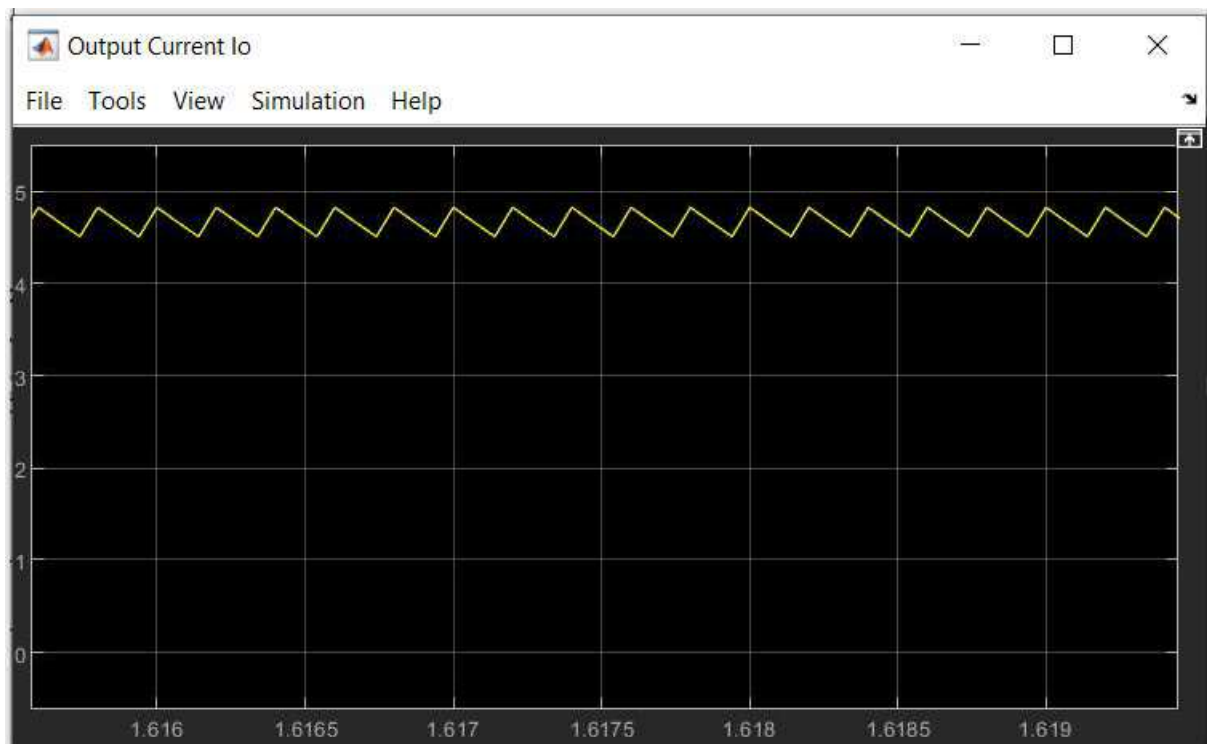


Fig 6 : Voltage across Switch

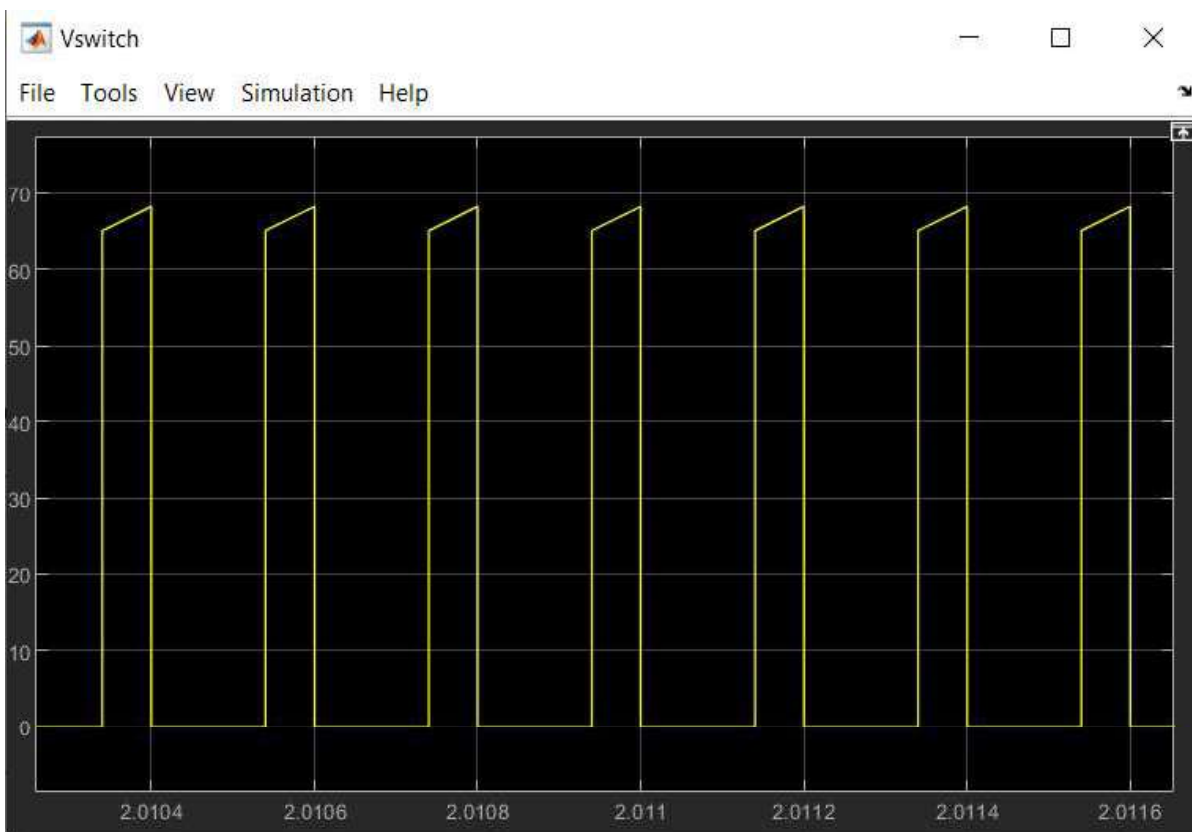


Fig 7 : Voltage across inductor (VL)

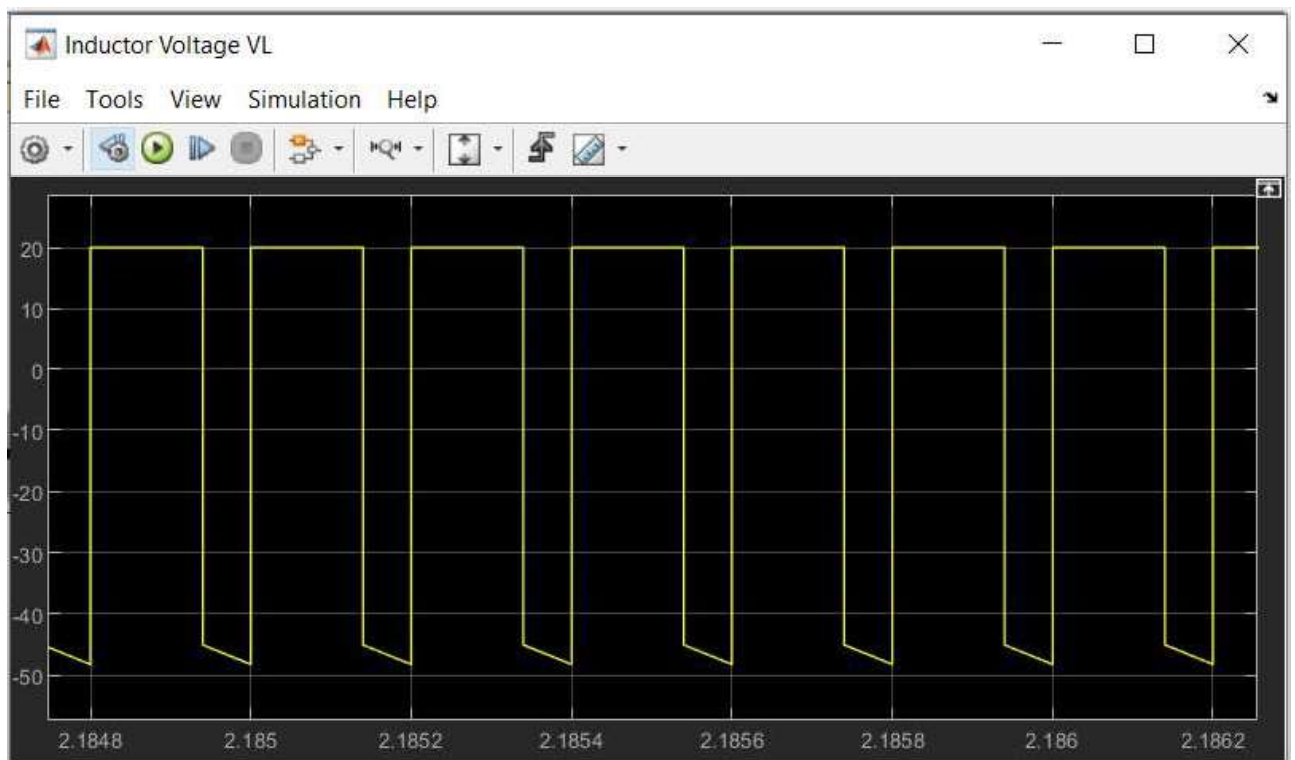


Fig 8 : Current through inductor (IL)

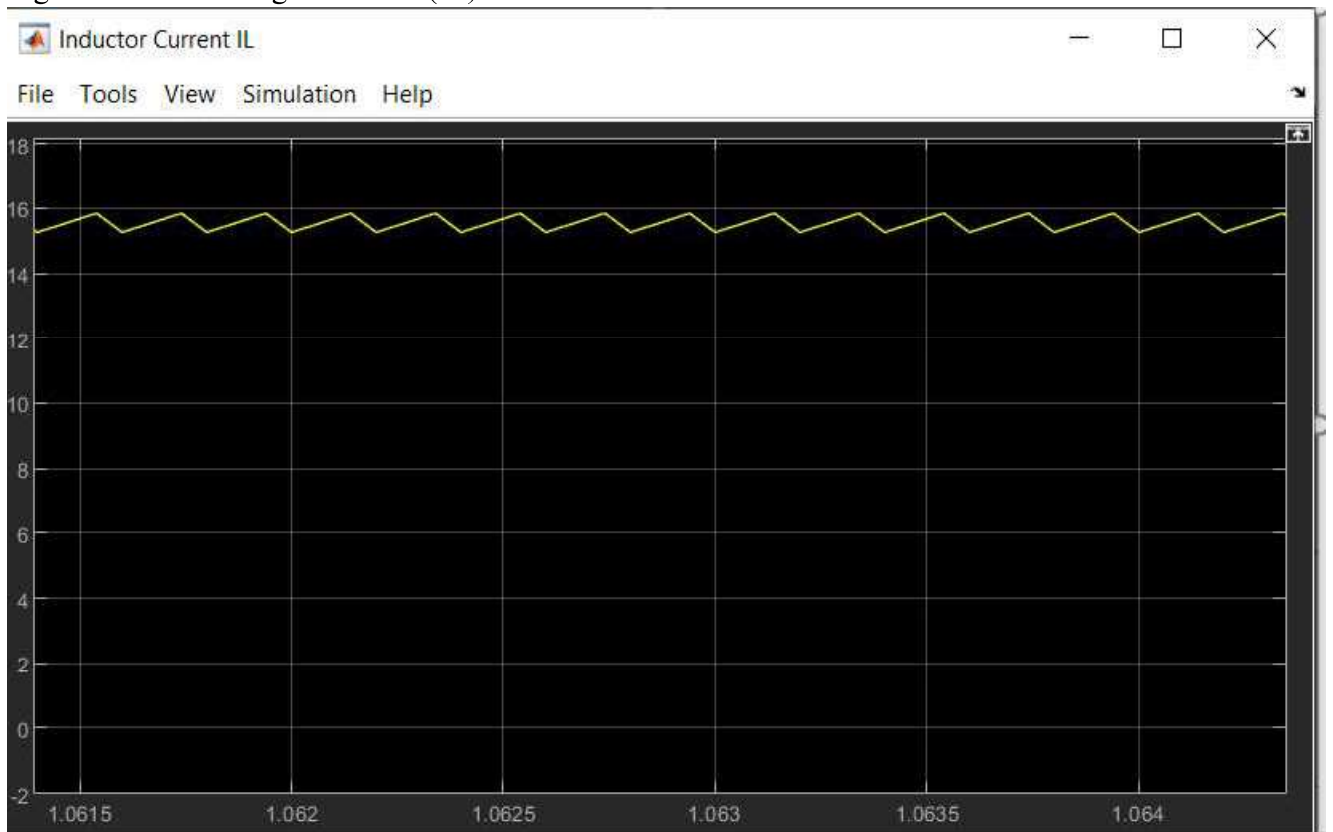


Fig 9 : Current through diode( $I_{\text{diode}}$ ) and Voltage across diode ( $V_{\text{diode}}$ )


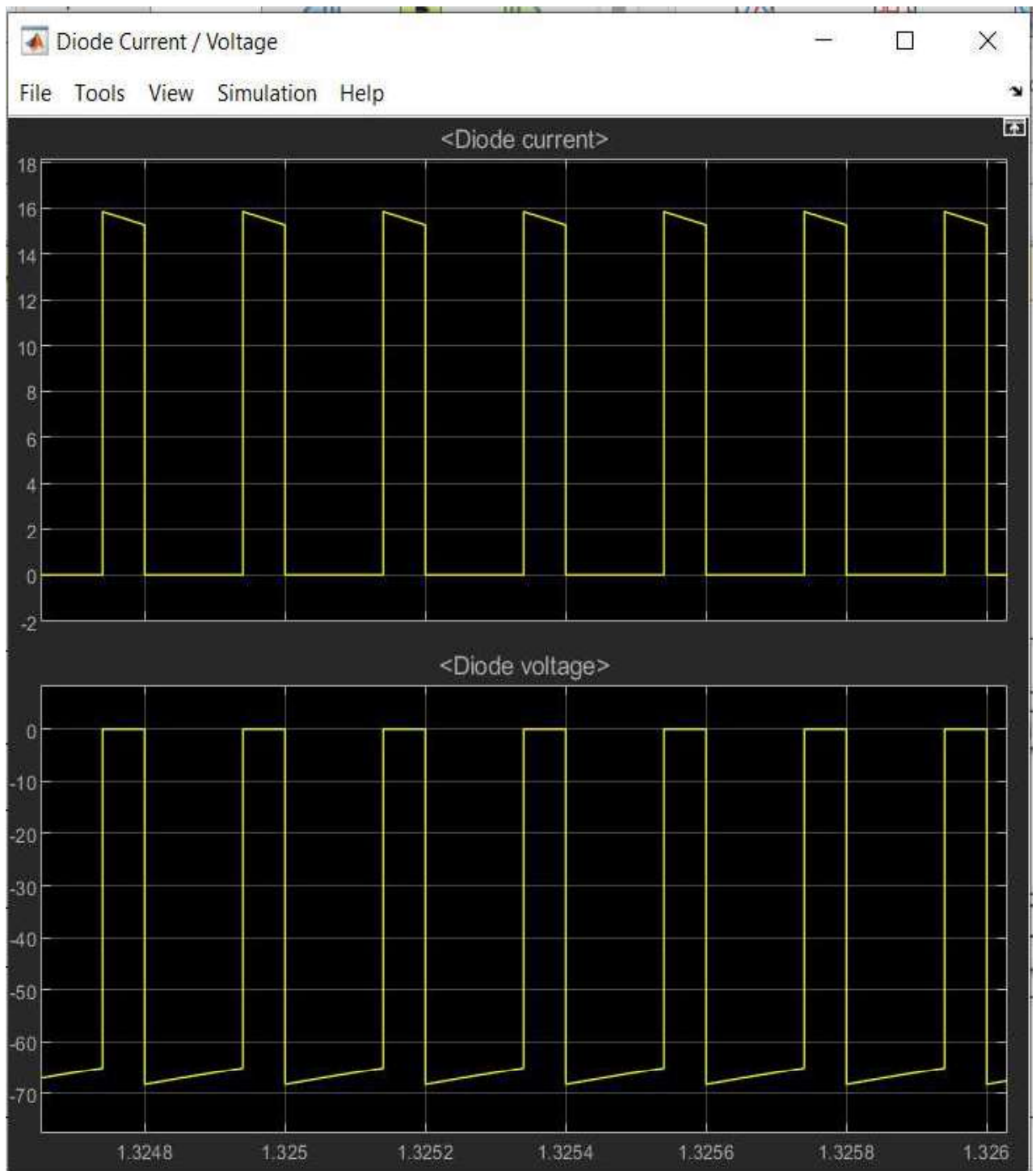


Fig 10 : Current through capacitor ( $I_c$ )

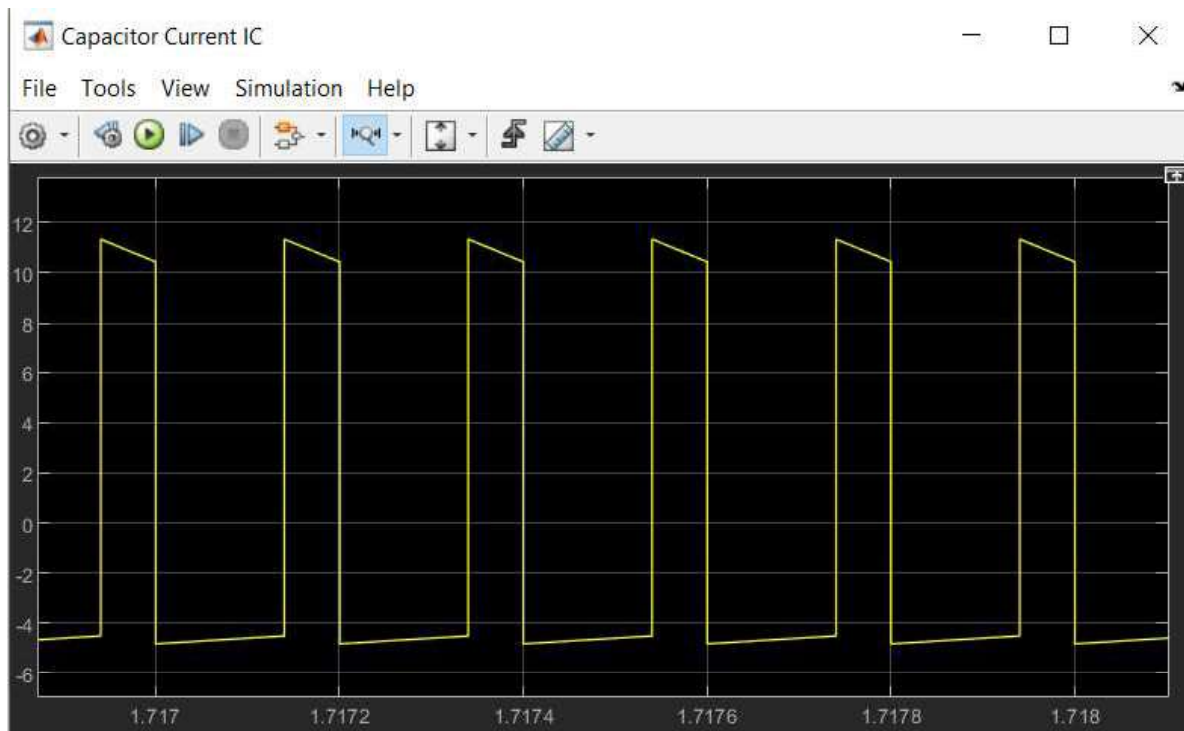

## Conclusion :

Buck-Boost converter is simulated in Matlab as buck converter is visualized with  $d=0.3$  and boost converter is visualized with  $d=0.7$  and output waveforms are obtained.